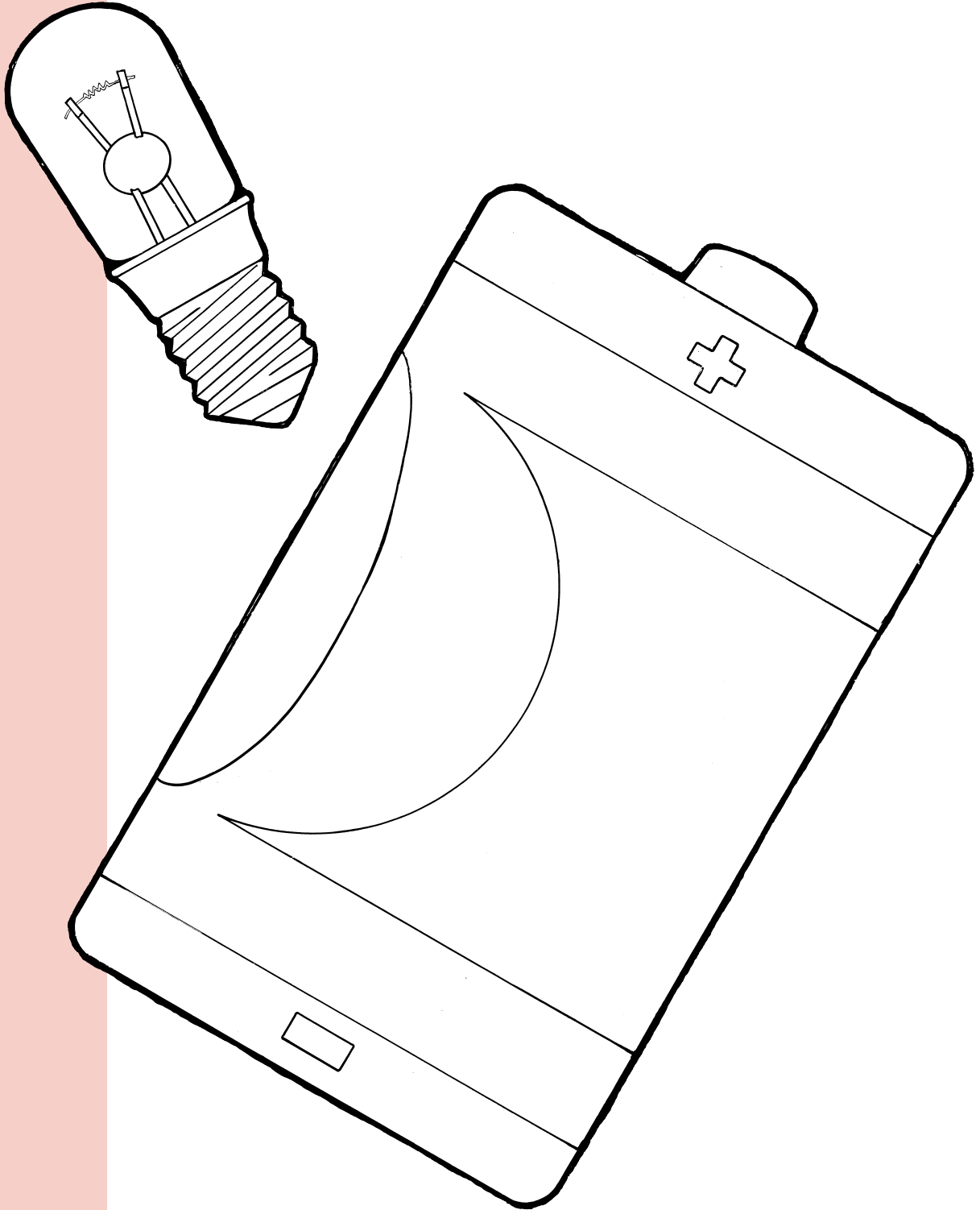


**Figure 3-1**

*D-cell and bulb*












Activity Sheet 1

Name: \_\_\_\_\_

Date: \_\_\_\_\_

Will the bulb light or not? Below each picture, make your prediction by writing either "On" or "Off."

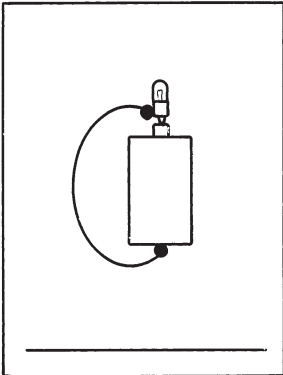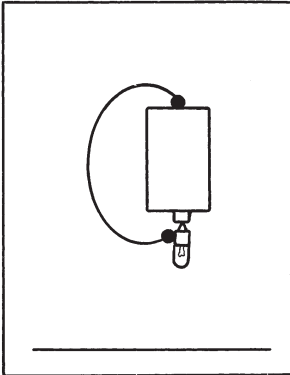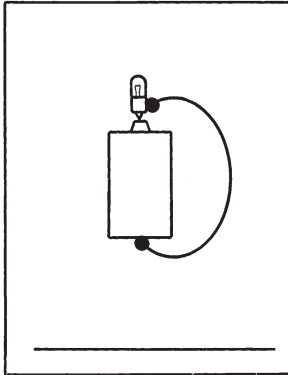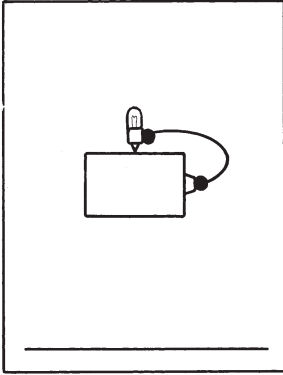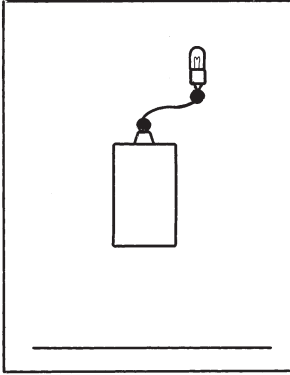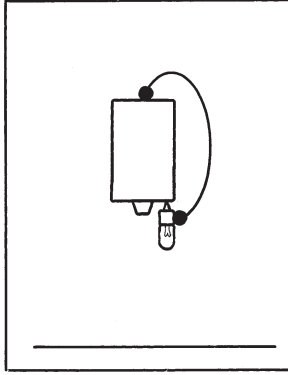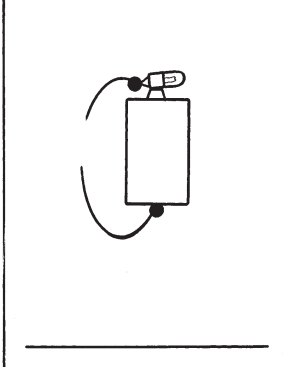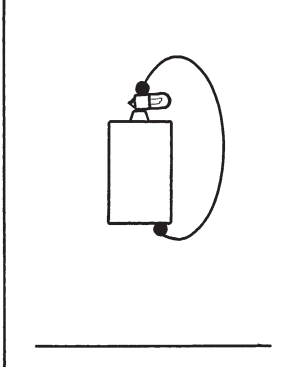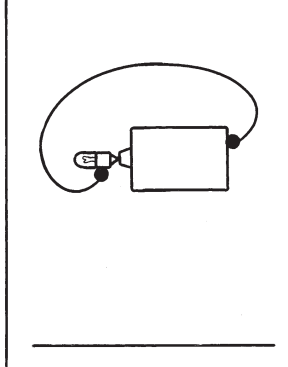 <p>_____</p>	 <p>_____</p>	 <p>_____</p>
 <p>_____</p>	 <p>_____</p>	 <p>_____</p>
 <p>_____</p>	 <p>_____</p>	 <p>_____</p>