

Name: _____

Date: _____

First, draw one more wire on the top two pictures so that the bulb will light. Then complete the partially drawn wires in the bottom two pictures to make a complete circuit, which will light the bulb.

